

## Structural Design in HDL


### 1. Lab Description

#### Part A: Half Adder


Students are asked to design a 1-bit half adder using HDL. Use the port names based on the picture shown below. Write a testbench code to verify your design.

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Truth table

 


Schematic

 

Realization

 
#### Part B: Full Adder

Using the half adder designed in Part A implement a 1-bit full adder circuit. Verify your design by writing a testbench code


 
#### Part C: 4-Bit Ripple Carry Adder

Using the Full Adder designed in Part B create a 4-bit ripple carry adder.



---

Write your answers from here.

**A. Half Adder**

**Code:**

```
module HalfAdder(A, B, Sum, Carry);  
    input A,B;  
    output Sum,Carry;  
  
    assign Sum = A ^ B;  
    assign Carry = A & B;  
  
endmodule
```

**Test Bench:**

```
module HalfAdder_HalfAdder_TB_v_tf();  
  
    // DATE: 21:22:33 09/17/2018  
    // MODULE: HalfAdder  
    // DESIGN: HalfAdder  
    // FILENAME: HalfAdder_TB.v  
    // PROJECT: EGCP450_Lab2  
    // VERSION:  
  
    // Inputs  
    reg A;  
    reg B;  
  
    // Outputs  
    wire Sum;  
    wire Carry;  
    // Bidirs  
  
    // Instantiate the UUT  
    HalfAdder uut (  
        .A(A),  
        .B(B),  
        .Sum(Sum),  
        .Carry(Carry)  
    );  
  
    // Initialize Inputs
```

```

initial begin
    A = 0;
    B = 0;

    #10;
    A = 0;

    B = 1;

    #10;
    A = 1;

    B = 0;

    #10;
    A = 1;


    B = 1;

    #10;

end
endmodule

```

### Wave:

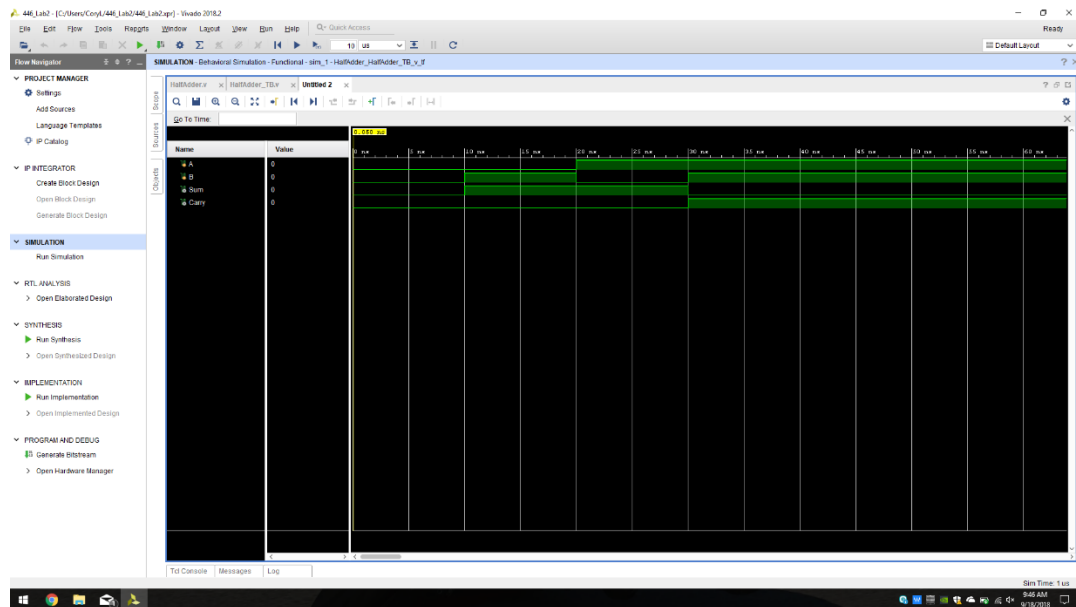

**Test Bench:**

```
module FullAdder_FullAdder_TB_v_tf();
```

```
// DATE: 21:24:44 09/17/2018
```

```
// MODULE: FullAdder
```

```
// DESIGN: FullAdder
```

```
// FILENAME: FullAdder_TB.v
```

```
// PROJECT: EGCP450_Lab2
```

```
// VERSION:
```

```
// Inputs
```

```
reg A;
```

```
reg B;
```

```
reg Cin;
```

```
// Outputs
```

```
wire Sum;
```

```
wire Cout;
```

```
// Bidirs
```

```
// Instantiate the UUT
```

```
FullAdder uut (
```

```
    .A(A),
```

```
    .B(B),
```

```
    .Cin(Cin),
```

```
    .Sum(Sum),
```

```
    .Cout(Cout)
```

```
);
```

```
// Initialize Inputs
```

```
initial begin
```

```
    A = 0;
```

```
    B = 0;
```

```
    Cin = 0;
```

```
    #10;
```

```
    A = 0;
```

```
    B = 1;
```

```
    #10;
```

```
    A = 1;
```

```
    B = 0;
```

```
    #10;
```

```
    A = 1;
```


```

        B = 1;
        #10;
    end

endmodule

```

### Wave:

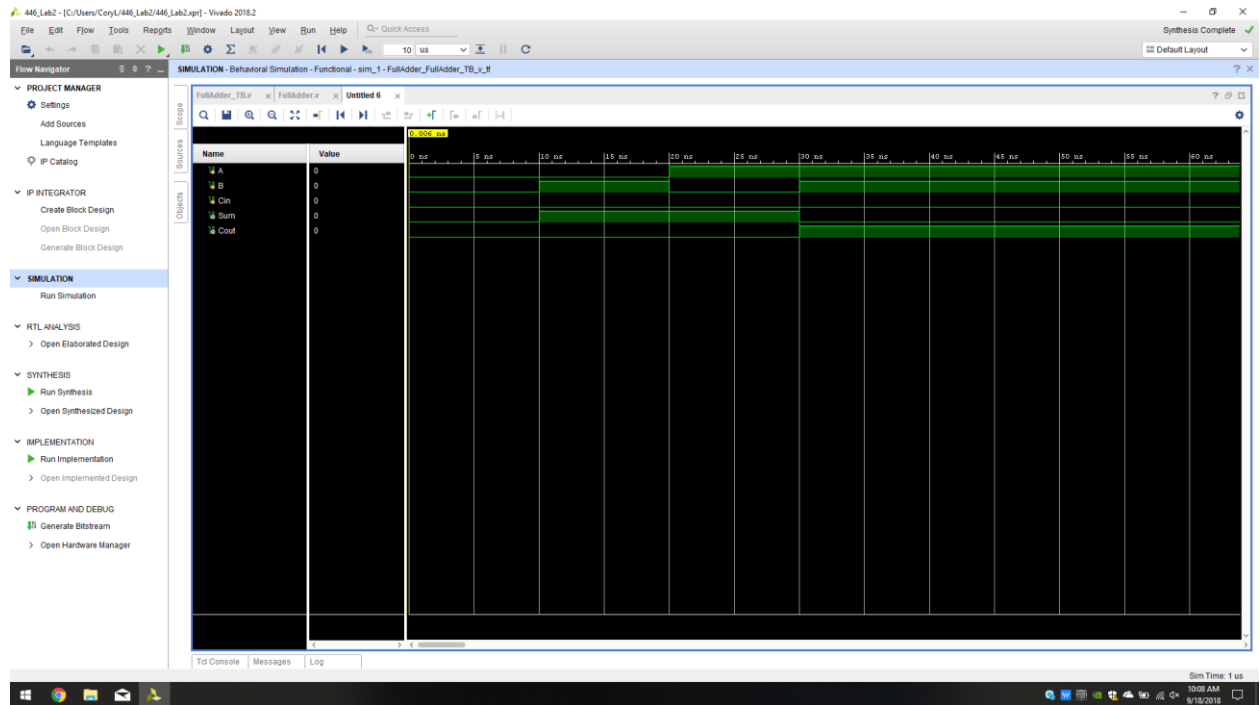

### C. 4-Bit Ripple Carry Adder

#### Code:

```
module RippleCarryAdder(A, B, Cin, Sum, Cout);
```

```
    input [3:0] A, B;
```

```
    input Cin;
```

```
    output [3:0] Sum;
```

```
    output Cout;
```

```
    wire [2:0] C;
```

```
    FullAdder
```

```
        FA0 (.A(A[0]), .B(B[0]), .Cin(Cin), .Cout(C[0]), .Sum(Sum[0]) ),
```

```
        FA1 (.A(A[1]), .B(B[1]), .Cin(C[0]), .Cout(C[1]), .Sum(Sum[1]) ),
```

```
        FA2 (.A(A[2]), .B(B[2]), .Cin(C[1]), .Cout(C[2]), .Sum(Sum[2]) ),
```

```
        FA3 (.A(A[3]), .B(B[3]), .Cin(C[2]), .Cout(Cout), .Sum(Sum[3]) );
```

```
endmodule
```