

- 6.15 Write a behavioral architecture declaration for the DFF shown in Figure P6.15. Use an if statement and an elsif statement. The signal *SET* (asyn) is clock independent—that is, it overrides the clock.

 


FIGURE P6.15

- 6.44 Write a dataflow architecture declaration for the counter circuit in Figure P6.44. Use three conditional signal assignments. The signal *INIT* (asyn) is clock independent—that is, it overrides the clock.

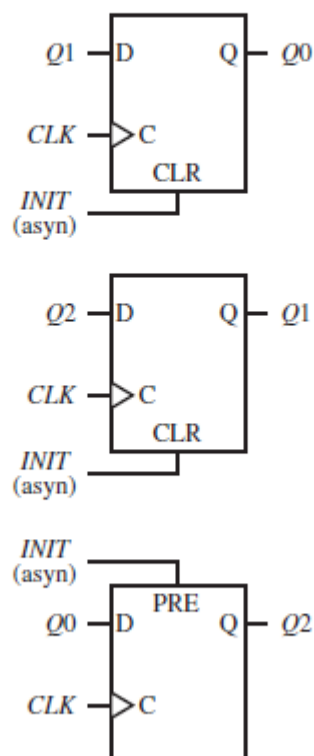


FIGURE P6.44

- 6.45 Write the required library clause, use clause (for the package IEEE.STD_LOGIC_1164), and entity declaration for the counter circuit in problem 6.44.

- 6.46** Combine your code for problems 6.44 and 6.45 to form a complete VHDL design. Obtain a waveform diagram that shows correct functionality for the complete VHDL design.
- 6.59** Use the arithmetic method to write a behavioral architecture declaration with a process for a binary up counter that increment by 2 as shown in Figure P6.59. The signal *RST* (asyn) is clock independent—that is, it overrides the clock.

 


FIGURE P6.59

- 6.60** Write the required library clause, use clauses, and entity declaration for the counter in problem 6.59.
- 6.61** Combine your code for problems 6.59 and 6.60 to form a complete VHDL design. Obtain a waveform diagram that shows correct functionality for the complete VHDL design.
- 6.67** For a crystal clock oscillator frequency of 100 MHz, how many clock cycles must be counted for each half-period to generate an accurate frequency of 10 Hz and also an accurate frequency of 4 Hz?
- 6.70** Use the PS/NS tabular method to write a behavioral architecture declaration for the counter shown in Figure P6.70. The signal *SET* (syn) is clock dependent—that is, it doesn't take effect until the clock ticks.

 


FIGURE P6.70

- 6.71** Write the required library clause, use clause (for the package IEEE.STD_LOGIC_1164), and entity declaration for the counter in problem 6.70.
- 6.72** Combine your code for problems 6.70 and 6.71 to form a complete VHDL design. Obtain a waveform diagram that shows correct functionality for the complete VHDL design.